

The Von Neumann Model Internals —Computer Organization—

Lionel Morel

Computer Science and Information Technologies - INSA Lyon

Fall-Winter 2024-25

The micro-machine ISA (1/3)

In the first lab sessions, we'll look at a home-made processor.

- ▶ 8-bits instructions
- ▶ 8-bits signed integers only
- ▶ 2 8-bits registers, named A and B

Computation instructions with 1 or 2 operands

```
B -> A          21 -> B
B + A -> A       B xor -42 ->
                  A
not B -> A       lsr A -> A
A xor 12 -> A    B - A -> A;
```

WARNING: some instructions that would seem “intuitive” are actually forbidden... eg: $A+B \rightarrow B$ is incorrect ... $B+A \rightarrow B$ is correct.

The micro-machine ISA (2/3)

Memory reads and writes

$*A \rightarrow A$	$*A \rightarrow B$
$A \rightarrow *A$	$B \rightarrow *A$
$*cst \rightarrow A$	$*cst \rightarrow B$
$A \rightarrow *cst$	$B \rightarrow *cst$

***A means: “the content of memory at the address contained in register A”.**

The micro-machine ISA (3/3)

Unconditional absolute branch

JA 42

continues execution at address 42.

Conditional relative branch

JR offset

JR offset IFZ

(executed if Z=1)

JR offset IFC

JR offset IFN


(executed if C=1)

(executed if N=1)


The micro-machine ISA - example program

```
prog2: *21 -> A    ;; copy Mem[21] to register A
      *42 -> B    ;; copy Mem[42] to register B
      B+A -> B    ;; Compute B+A and put result
                      ;; into register B
      B -> *43    ;; copy content of register B to Mem[43]
```

 
Von Neumann Architecture (from last time)



Von Neumann Architecture (refined)

 


1- Execute Instructions

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

1- Execute Instructions

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

1- Execute Instructions

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

1- Execute Instructions

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

1- Execute Instructions

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

1- Execute Instructions

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

1- Execute Instructions

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

1- Execute Instructions

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

1- Execute Instructions

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

2- Advance in Program

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

2- Advance in Program

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

2- Advance in Program

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

2- Advance in Program

 


MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

2- Advance in Program

 

MA: Memory Address
MDO: Memory Data Output
MDI: Memory Data Input
ceM: clock-enable Memory (needs 1 when writing TO memory)

DataPath - The Big Picture

 


Instruction Encoding


The **IR** register contains a **binary encoding** of the instruction being executed.

msp430


- ▶ 2 operands instructions

 

- ▶ 1 operand instructions

 


- ▶ jumps

 

micro-machine

bit	7	6	
instruction autres que JR	0		cc
saut relatif conditionnel	1		cond, vo


The Control Unit

 

- ▶ Implements the passing from one instruction to the next
- ▶ Manipulates registers through “Chip Enable” commands: **ceRegA**, **ceRegB**, **cePC**, **ceIR**, etc.
- ▶ Manipulates memory through control signals: **ceM**
- ▶ Performs selection over data to be written to registers or buses: **JR**, **JA**, **progFetch**, etc.


Control Unit

 The Control Unit is an Algorithmic State Machine (see Guillaume Beslon's lectures)



- ▶ F is the **Output** function
- ▶ T is the **Transition** function
- ▶ F and T are **combinatorial** circuits (no registers)

Von Neumann's Control Unit - Interface

 

Executing Programs - The Von Neumann Cycle

Given the structure of a program in a Von Neumann's machine, the algorithm to execute it is simple:

Do forever:

Fetch Instruction

Decode Instruction

Execute Instruction

A Von Neumann machine is an ASM¹ that executes this **Von Neumann Cycle** such that:

Fetch Copy the current instruction bit-vector from the memory to the processor (register IR)

Decode Look at the instruction opcode to prepare the DataPath

Execute Process the data in the DataPath such that the processor **makes the behavior of the instruction happen**

!! Don't forget to move to the "next" instruction

¹ASM = Abstract State Machine ... different from ASM/asm for "assembler"

The Micro-machine


B -> A	21 -> B
B + A -> A	B - A?
not B -> A	lsr A -> A
A xor 12 -> A	B - A -> A
B xor -42 -> A	

*A -> A	*A -> B
A -> *A	B -> *A
*cst -> A	*cst -> B
A -> *cst	B -> *cst


JA 42

JR offset	JR offset IFZ <i>(executed if Z=1)</i>
JR offset IFC <i>(executed if C=1)</i>	JR offset IFN <i>(executed if N=1)</i>



The VN's automaton - Fetch-Decode

 

The VN's automaton - Fetch-Decode

 

 
 
The VN's automaton - Arithmetic/Logic ins on 1 byte



$B + A \rightarrow A$

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	0	0	0	0	1	0

 
 
The VN's automaton - Arithmetic/Logic ins on 1 byte



$B + A \rightarrow A$

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	0	0	0	0	1	0

 
 
The VN's automaton - Arithmetic/Logic ins on 1 byte



$B + A \rightarrow A$

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	0	0	0	0	1	0



The VN's automaton - Comparison

  

B - A?

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	0	0	0	0	1	α



The VN's automaton - Comparison

  

B - A?

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	0	0	0	0	1	α



The VN's automaton - Comparison

  

B - A?

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	0	0	0	0	1	α

 
 
The VN's automaton - Conditional relative jumps



JR -5 IFN

bit	7	6	5	4	3	2	1	0
saut relatif conditionnel	1	cond		offset signé sur 5 bits				
	1	1	1	1	1	0	1	1

  
The VN's automaton - Conditional relative jumps



JR -5 IFN


bit	7	6	5	4	3	2	1	0
saut relatif conditionnel	1	cond		offset signé sur 5 bits				
	1	1	1	1	1	0	1	1

 The VN's automaton - Conditional relative jumps




If condition is true (ie take the jump)

JR -5 IFN

 


bit	7	6	5	4	3	2	1	0
saut relatif conditionnel	1	cond		offset signé sur 5 bits				
	1	1	1	1	1	0	1	1

 The VN's automaton - Conditional relative jumps



If condition is false (ie DON'T take the jump)

JR -5 IFN

 

bit	7	6	5	4	3	2	1	0
saut relatif conditionnel	1	cond		offset signé sur 5 bits				
	1	1	1	1	1	0	1	1

Computing “conditions”

The automaton uses the `JumpCondTrue` for testing if a relative jump should be taken.

This signal needs to be computed from:



- ▶ flags (Z, C, N) which represent
- ▶ the instruction's condition (IFZ, IFC, IFN, ... or none).

We want to **take the jump** if the “correct combination” occurs:

- ▶ `Z==1` and instruction's condition is IFZ (`cond==01`)
- ▶ `C==1` and instruction's condition is IFC (`cond==10`)
- ▶ `N==1` and instruction's condition is IFN (`cond==11`)
- ▶ the instruction jumps **inconditionnally** (`cond==00`)

TODO: build the small combinatorial circuit that computes `JumpCondTrue` from `flags` and `cond`

 
 
The VN's automaton - 2-bytes instructions



A xor 12 -> A

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	1	0	0	1	0	0
constante encodée sur 8 bits	0	0	0	0	1	1	0	0

 
 
The VN's automaton - 2-bytes instructions



A xor 12 -> A

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	1	0	0	1	0	0
constante encodée sur 8 bits	0	0	0	0	1	1	0	0

 
 
The VN's automaton - 2-bytes instructions



A xor 12 -> A

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	1	0	0	1	0	0
constante encodée sur 8 bits	0	0	0	0	1	1	0	0

 
 
The VN's automaton - 2-bytes instructions



A xor 12 -> A

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	1	0	0	1	0	0
constante encodée sur 8 bits	0	0	0	0	1	1	0	0



The VN's automaton - Memory reads

  

***A -> B**

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	1	0	0	1	0	0



The VN's automaton - Memory writes

  

B -> *A

B -> *200

The VN's automaton - Absolute Jumps

  

JA 42

bit	7	6	5	4	3	2	1	0
instruction autres que JR	0	codeop				arg2S	arg1S	destS
	0	0	1	0	0	1	0	0
constante encodée sur 8 bits	0	0	1	0	1	0	1	0

Outline


Sign Extension

Byte-order

(A bit) more advanced topics

Sign Extension

 - Some instructions manipulate data encoded on different numbers of bits



Outline

Sign Extension

Byte-order

(A bit) more advanced topics

Byte-order: Definitions (1)

- By convention, a computer will store in memory bytes of a data word in a given order.

Definition 1: Big-endianness

$\triangleq$ *convention by which a computer stores bytes of a number in memory from the most-significant byte (at the smallest address) to the least-significant byte (at the highest address). Such a computer is called **big-endian**.*

Byte-order: Definitions (2)

Definition 2: Little-endianness


$\triangleq$ *convention by which a computer stores bytes of a number in memory from the less-significant byte (at the smallest address) to the most-significant byte (at the highest address). Such a computer is called **little-endian**.*

Byte-order: Example

one 32-bit integer

0A0B0C0D

arranged as
four bytes in
memory

 


Little-endian

arranged as
four bytes in
memory

one 32-bit integer

0A0B0C0D

 

Big-endian

Outline

Sign Extension

Byte-order

(A bit) more advanced topics

(A bit) more advanced topics

Un-Pipelined Execution

The behavior of the processor (Fetch/Decode/execute) can be refined:

IF : Instruction Fetch

- ▶ Copy instruction word from memory to IR

ID : Instruction Decode

- ▶ Prepare operands
- ▶ JA 10: read constant from memory
- ▶ JR +3 IFN: extend 5-bits +3 to 8-bits

EX : Execute

- ▶ Send correct control signal to ALU
- ▶ Let arguments run towards ALU

MEM : Write/Read stuff to/from memory


- ▶ A $\rightarrow$ *42
- ▶ copy the current value of register A into memory at address 42.

WB : Writeback (result to register)

- ▶ Write value out of ALU into target register

Un-Pipelined Execution

 Until now, the execution of n instructions looks like this:



- ▶ If each step takes δns ,
- ▶ Then 1 instruction takes $5 * \delta ns$,
- ▶ Then **n instructions take $\underline{n * 5 * \delta ns}$** to execute (ouch!).

Pipeline - Principle


- ▶ **Steps are independent** from one another
- ▶ Each step (IF, ID, EX, MEM, WB) can be realized with a **distinct part of the datapath**
- ▶ Data can move from one stage of the datapath to the next with **no delay**

The Processor datapath can work like an **Assembly Line**



Pipelined Execution

 Now, the execution of the same n instructions looks like this:



- ▶ If each steps takes δ ns, then **n instructions take**
 $5 * \delta + (n - 1) * \delta = (\mathbf{n + 4}) * \delta$ **ns**
to execute.
- ▶ Expected gain: Processor gets D times faster (where D is the Depth of the pipeline).
- ▶ In nominal mode of course (see pipeline hazards)


Pipelined Execution

What's the implication on the processor design?

- ▶ The pipeline stages are separate parts of the CPU
- ▶ They are organized so that each stage takes one instruction at each new clock cycle
- ▶ An instruction is “passed” from one stage to the next




 Un-pipelined versus pipelined architecture (1/2)



NB: This is taken from D. A. Patterson, & J. L. Hennessy, *Computer Organization and Design*, p265. You should convince yourself that our micro-machine is **very close** to this. See also https://en.wikipedia.org/wiki/MIPS_architecture

 Un-pipelined versus pipelined architecture (2/2)



- ▶ Each **blue line** corresponds to a set of **stage-specific registers**
- ▶ eg IF/ID = info produced by Instruction Fetch, and needed by Instruction Decode.
- ▶ These are used to store data that needs to be passed from one stage to the next
- ▶ NB: control signals are missing!!


Pipeline hazards

The pipeline's behavior may be disrupted by the following:


- ▶ **Structural hazard**: two instructions in different stages of the pipeline require the same resource.
- ▶ **Data hazard**: the data required by an instruction was not already produced by a preceding instruction.
- ▶ **Control hazard**: an instruction execution is interrupted, typically by a branch.

- ▶ The general solution consists in inserting **bubbles** into the pipeline.
- ▶ This amounts to adding **NOPs**, ie “**do-nothing instructions**” into the program.

Pipeline hazards

 


Pipeline hazards

 

1. Structural Hazard

Both $A \rightarrow *42$ and $B+A \rightarrow B$ require memory simultaneously. We need to **delay 2nd instruction.**


Pipeline hazards

 

1. Structural Hazard

Both A->*42 and B+A->B require memory simultaneously. We need to **delay 2nd instruction.**

Pipeline hazards

 


2. Data Hazard

B+A->B can only be executed correctly when A+2->A is fully finished, ie we need to wait for the value of A to be fully updated.

NB: no structural hazard here because B+1->B doesn't use the MEM stage.

Pipeline hazards

 


2. Data Hazard


B+A->B can only be executed correctly when A+2->A is fully finished, ie we need to wait for the value of A to be fully updated.

NB: no structural hazard here because B+1->B doesn't use the MEM stage.

Pipeline hazards

 


Pipeline hazards

 

3. Control Hazard

The control flow associated to instruction `BR +3 IFN` can only be evaluated when **B** is fully updated by previous instruction.

Pipeline hazards

 

3. Control Hazard

The control flow associated to instruction BR +3 IFN can only be evaluated when **B** is fully updated by previous instruction.

Other sources of optimization (1/2)

Inside the CPU

These are advanced topics, not addressed in AO. Got and check'em out if you are interested.

- ▶ Superscalar²: A **superscalar processor** executes multiple instructions in parallel by using multiple execution units (eg several ALUs), whereas the latter (pipeline) executes multiple instructions in the same execution unit in parallel by dividing the execution unit into different phases
- ▶ Very-Large Instruction Words³: A **VLIW processor** allows programs to explicitly specify instructions to execute in parallel
- ▶ support for multi-threading

²https://en.wikipedia.org/wiki/Superscalar_processor

³https://en.wikipedia.org/wiki/Very_long_instruction_word

Other sources of optimization (2/2)

Outside the CPU

- ▶ multi-core
- ▶ many-core, GPUs, etc.