

Combinatorial circuits - arithmetics

Lecturer: Guillaume Beslon
(Lecture adapted from Lionel Morel)

Computer Science and Information Technologies - INSA Lyon

Fall 2024

Blackboard:
How to add two integers?

Half-Adder

The simplest one-bit operation used is called a *half adder* :


- ▶ inputs : two bits a and b that we want to add;
- ▶ outputs : a sum bit s and an output carry c_o .

a	b	s	c_o
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

We see that:

$$s = a \oplus b, \quad \text{et} \quad c_o = a \cdot b.$$

We build the corresponding circuit:

 

Ah! But we also need to take the input carry into account.

Blackboard

Full-Adder

The *full adder* has:

- ▶ inputs: 2 bits a and b , and one bit for the incoming carry c_i ;
- ▶ outputs: one bit for the sum s and one bit for the output carry c_o .

a	b	c_i	s	c_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

We see that:

$$s = \bar{a}(b \oplus c_i) + a(\overline{b \oplus c_i}).$$

Since $x \oplus y = \bar{x}y + x\bar{y}$, we get


$$s = a \oplus (b \oplus c_i) = a \oplus b \oplus c_i.$$

For the carry:

$$\begin{aligned}c_o &= \bar{a}bc_i + a\bar{b}c_i + ab\bar{c}_i + abc_i \\ &= (\bar{a}b + a\bar{b})c_i + ab(\bar{c}_i + c_i) \\ &= (a \oplus b)c_i + ab.\end{aligned}$$


Full-Adder (contd)

 We get the circuit for a 1-bit *full adder* :



n-bits Adder

 We can now cascade k full adders to build a circuit that adds up 2 k -bits natural numbers.



NB: The carry is propagated exactly as we do in the hand-written operation.

Blackboard: From addition to subtraction

Optimization criteria

A boolean function f can be implemented by many ($\rightarrow \infty$) circuits.

What choice criteria can we use?

- ▶ **number of logical gates** \rightarrow circuit (die) area
- ▶ **delay** \rightarrow circuit frequency
- ▶ **power consumption**

Optimization algorithms are exponential (in the number of input variables) \rightarrow an optimal circuit might not be found in a practicable time.

Example: Let's see how we can reduce a circuit's **delay** by parallelizing it.

Propagation Delay

Any circuit has a certain **Propagation delay** τ , defined as the time between a change on the circuit's inputs (at t) and the stabilization of the circuit's outputs (at $t + \tau$).

During $[t, t + \tau]$, outputs can be in **unpredictable transient states**.

Propagation Delay and Critical Path

Each logical gate has a given (physically-fixed) delay.


To determine a circuit's propagation delay, we need:

- ▶ compute the propagation delay associated to each path that connect one input to one output of the circuit;
- ▶ identify a path whose delay is maximal. This is called a **critical path**

A circuit's propagation delay = delay of one of its critical paths.

NB: There may be several critical paths.

Example¹

 




¹https://en.wikipedia.org/wiki/Propagation_delay

Carry Lookahead

With a hypothetical 1 t propag. delay for all logical gates, the *full adder's* delay is 3 t. And the delay from c_i to c_o is **2 t**.

For a 4-bits adder, the critical path is the one from c_i to c_o : delay = **8 t**.

For a 8-bits adder, delay is **16 t**.

   


⇒ Delay is proportional to the length of the carry propagation path.

Carry Lookahead

Speculate possible results:

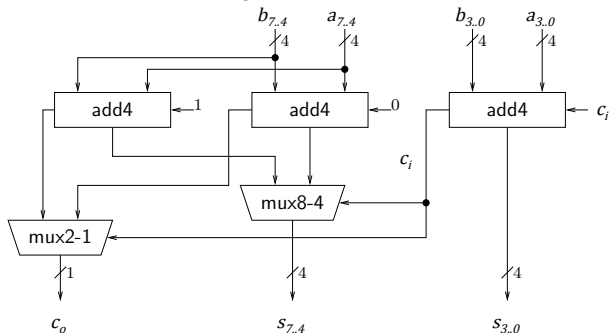- ▶ Compute the 4 LSbits of the result s , together with c_i
- ▶ In parallel, compute two versions of the 4 MSbits of s
 - ▶ One assuming that $c_i = 0$
 - ▶ One assuming that $c_i = 1$
- ▶ Choose $s_{7..4}$ according to c_i



Optimizing the (8-bits) adder

If mux have a $2t$ delay. After $8t$,

- ▶ c_i is known,
- ▶ the two versions (one for $c_i = 0$, one for $c_i = 1$)
- ▶ The selection can now occur, based on c_i .

Delay from c_i to c_o falls to c_i à c_o **$10t$** .

- ▶ We have just introduced **parallelism**.
- ▶ This reduces delay
- ▶ but it increases surface
- ▶ aka **space-time tradeoff**²....

²classic in CS, check out:

https://en.wikipedia.org/wiki/Space%E2%80%93time_tradeoff